

VINNITSA NATIONAL AGRARIAN UNIVERSITY

Department of General Engineering Sciences and Labour Safety



LAPLACE TRANSFORM. OPERATOR SUBSTITUTION SCHEMES

by Associate Professor V. Hraniak





Laplace transform. Operator substitution schemes

THE CONCEPT OF LAPLACE TRANSFORM

DEFINITION

- The Laplace transform is a linear operator that switched a function $f(t)$ to $F(s)$.

- Specifically:
$$F(s) = \mathcal{L}\{f(t)\} = \int_{0^-}^{\infty} e^{-st} f(t) dt.$$

where:

$$s = \sigma + i\omega.$$

- Go from time argument with real input to a complex angular frequency input which is complex.

RESTRICTIONS

- There are two governing factors that determine whether Laplace transforms can be used:
 - $f(t)$ must be at least piecewise continuous for $t \geq 0$
 - $|f(t)| \leq Me^{\gamma t}$ where M and γ are constants

CONTINUITY

- Since the general form of the Laplace transform is:

$$F(s) = \mathcal{L}\{f(t)\} = \int_{0^-}^{\infty} e^{-st} f(t) dt.$$

it makes sense that $f(t)$ must be at least piecewise continuous for $t \geq 0$.

- If $f(t)$ were very nasty, the integral would not be computable.

LAPLACE TRANSFORM THEORY

- General Theory

- Example

- Convergence

$$F(s) = \mathcal{L}(f(t)) = \int_0^{\infty} e^{-st} f(t) dt = \lim_{\tau \rightarrow \infty} \int_0^{\tau} e^{-st} f(t) dt$$

$$f(t) \equiv 1$$

$$\begin{aligned} \mathcal{L}(f(t)) &= \int_0^{\infty} e^{-st} 1 dt = \lim_{\tau \rightarrow \infty} \left(\frac{e^{-st}}{-s} \Big|_0^{\tau} \right) \\ &= \lim_{\tau \rightarrow \infty} \left(\frac{e^{-s\tau}}{-s} + \frac{1}{s} \right) = \frac{1}{s} \end{aligned}$$

$$f(t) \equiv e^{t^2}$$

$$\mathcal{L}(f(t)) = \lim_{\tau \rightarrow \infty} \int_0^{\tau} e^{-st} e^{t^2} dt = \lim_{\tau \rightarrow \infty} \int_0^{\tau} e^{t^2 - st} dt = \infty$$

LAPLACE TRANSFORMS

- Some Laplace Transforms
- Wide variety of function can be transformed
- Inverse Transform

$$\mathcal{L}^{-1}(F(s)) = f(t)$$

- Often requires partial fractions or other manipulation to find a form that is easy to apply the inverse

TABLE 6.2.1 Elementary Laplace Transforms

$f(t) = \mathcal{L}^{-1}\{F(s)\}$	$F(s) = \mathcal{L}\{f(t)\}$
1. 1	$\frac{1}{s}, \quad s > 0$
2. e^{at}	$\frac{1}{s-a}, \quad s > a$
3. $t^n, \quad n = \text{positive integer}$	$\frac{n!}{s^{n+1}}, \quad s > 0$
4. $t^p, \quad p > -1$	$\frac{\Gamma(p+1)}{s^{p+1}}, \quad s > 0$
5. $\sin at$	$\frac{a}{s^2+a^2}, \quad s > 0$
6. $\cos at$	$\frac{s}{s^2+a^2}, \quad s > 0$
7. $\sinh at$	$\frac{a}{s^2-a^2}, \quad s > a $
8. $\cosh at$	$\frac{s}{s^2-a^2}, \quad s > a $
9. $e^{at} \sin bt$	$\frac{b}{(s-a)^2+b^2}, \quad s > a$
10. $e^{at} \cos bt$	$\frac{s-a}{(s-a)^2+b^2}, \quad s > a$
11. $t^n e^{at}, \quad n = \text{positive integer}$	$\frac{n!}{(s-a)^{n+1}}, \quad s > a$
12. $u_c(t)$	$\frac{e^{-cs}}{s}, \quad s > 0$
13. $u_c(t)f(t-c)$	$e^{-cs}F(s)$
14. $e^{ct}f(t)$	$F(s-c)$
15. $f(ct)$	$\frac{1}{c}F\left(\frac{s}{c}\right), \quad c > 0$
16. $\int_0^t f(t-\tau)g(\tau) d\tau$	$F(s)G(s)$
17. $\delta(t-c)$	e^{-cs}
18. $f^{(n)}(t)$	$s^n F(s) - s^{n-1}f(0) - \dots - f^{(n-1)}(0)$
19. $(-t)^n f(t)$	$F^{(n)}(s)$

RESISTOR

- iv -relation in the time domain

$$v(t) = R \cdot i(t).$$

- By operational Laplace transform:

$$\begin{aligned} L\{v(t)\} &= L\{R \cdot i(t)\} = R \cdot L\{i(t)\} , \\ \Rightarrow V(s) &= R \cdot I(s). \end{aligned}$$

- Physical units: $V(s)$ in volt-seconds, $I(s)$ in ampere-seconds.

INDUCTOR

- i - v -relation in the time domain

$$v(t) = L \cdot \frac{d}{dt} i(t).$$

- By operational Laplace transform:


$$L\{v(t)\} = L\{L \cdot i'(t)\} = L \cdot L\{i'(t)\},$$

$$\Rightarrow V(s) = L \cdot [sI(s) - I_0] = sL \cdot I(s) - LI_0.$$

initial current

EQUIVALENT CIRCUIT OF AN INDUCTOR


■ Series equivalent:

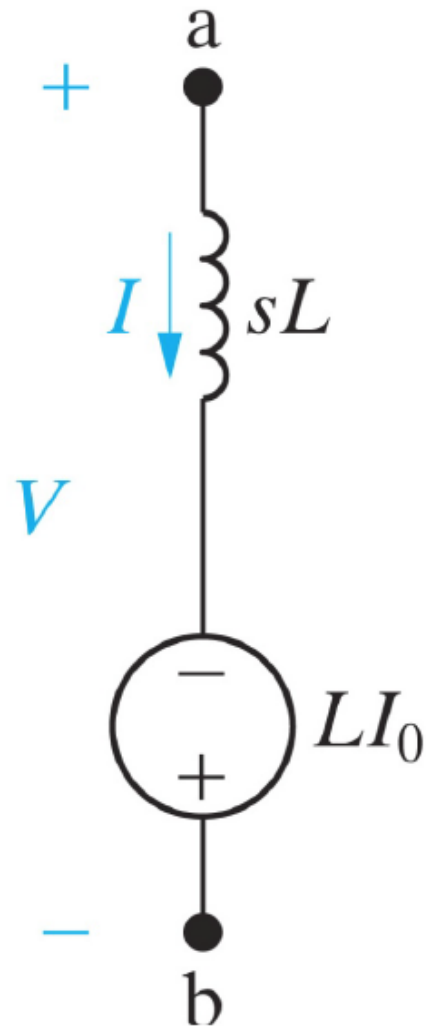

Thévenin →
Norton



■ Parallel equivalent:

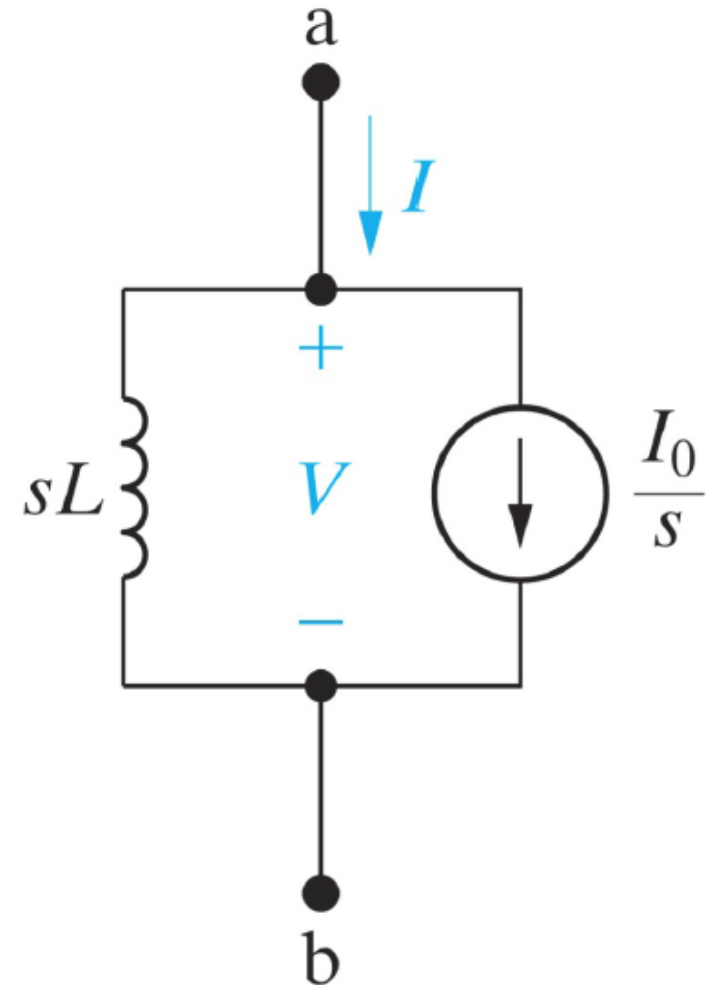

CAPACITOR

- i - v -relation in the time domain

$$i(t) = C \cdot \frac{d}{dt} v(t).$$

- By operational Laplace transform:


$$L\{i(t)\} = L\{C \cdot v'(t)\} = C \cdot L\{v'(t)\},$$

$$\Rightarrow I(s) = C \cdot [sV(s) - \overset{\circ}{V_0}] = sC \cdot V(s) - CV_0.$$


initial voltage

EQUIVALENT CIRCUIT OF A CAPACITOR

■ Parallel equivalent:

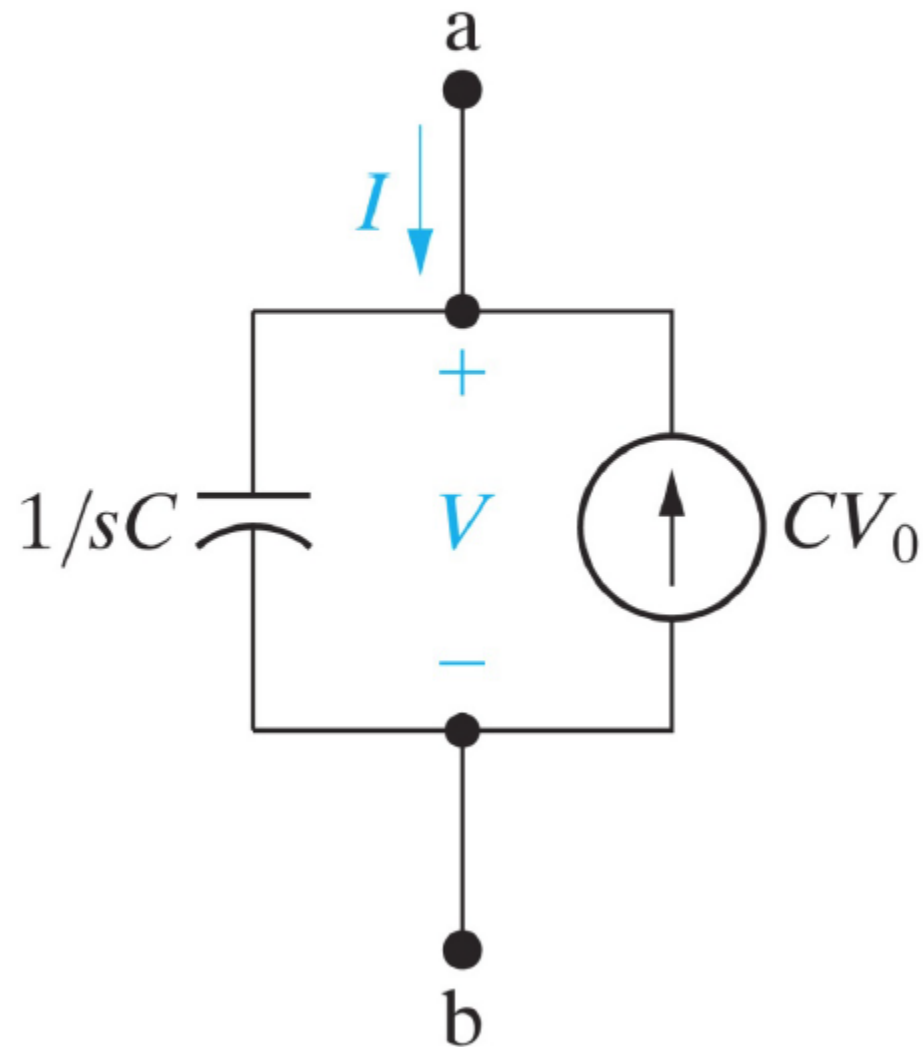

■ Series equivalent:

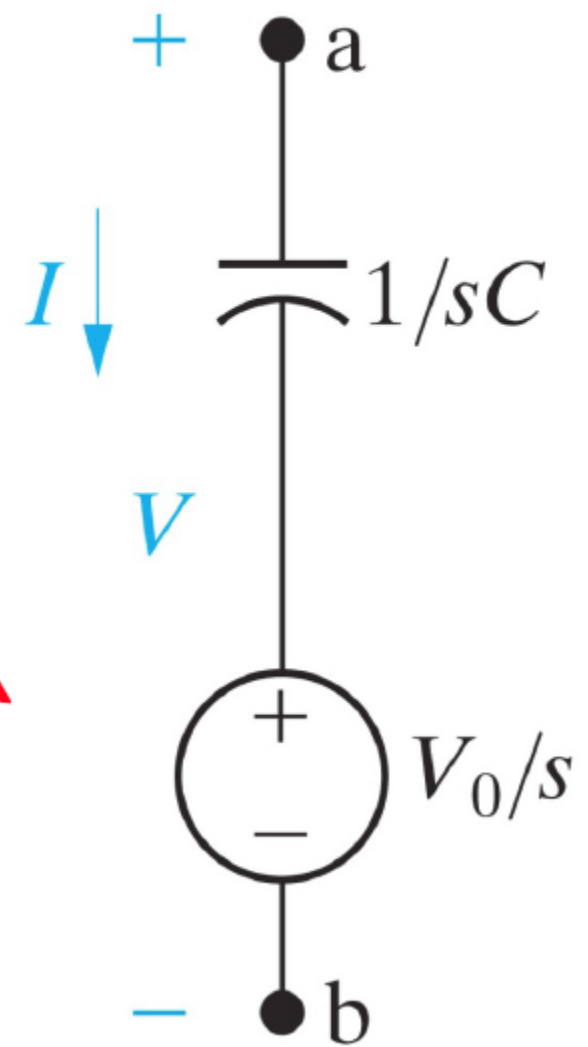


Norton →
Thévenin




AN EXAMPLE OF CONSTRUCTING AN OPERATOR SUBSTITUTION SCHEME

Original scheme

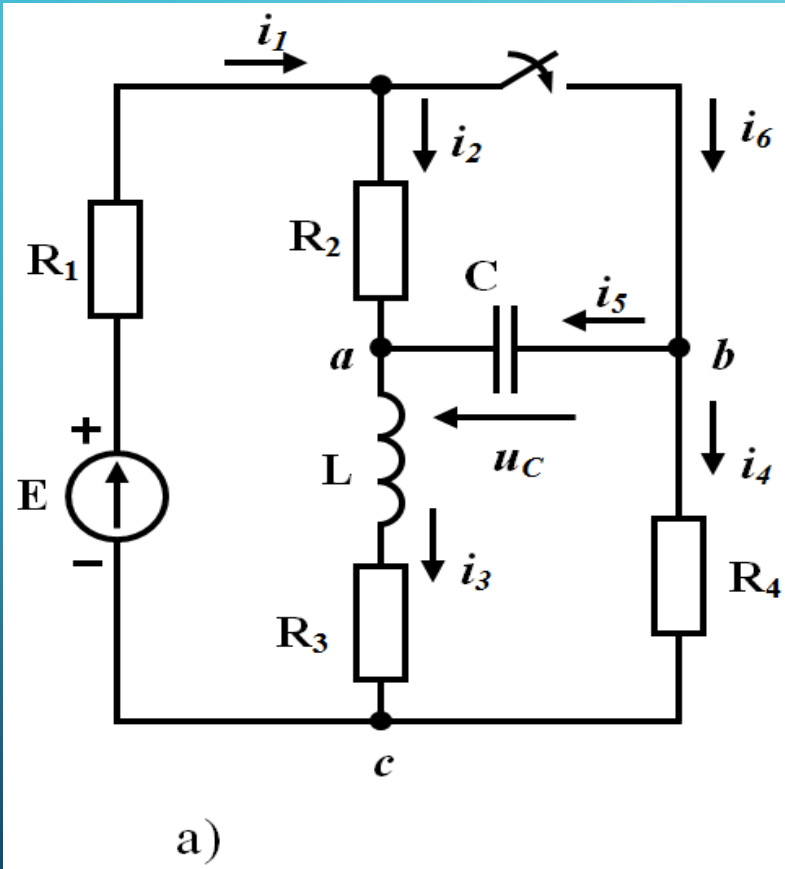

Substitution scheme

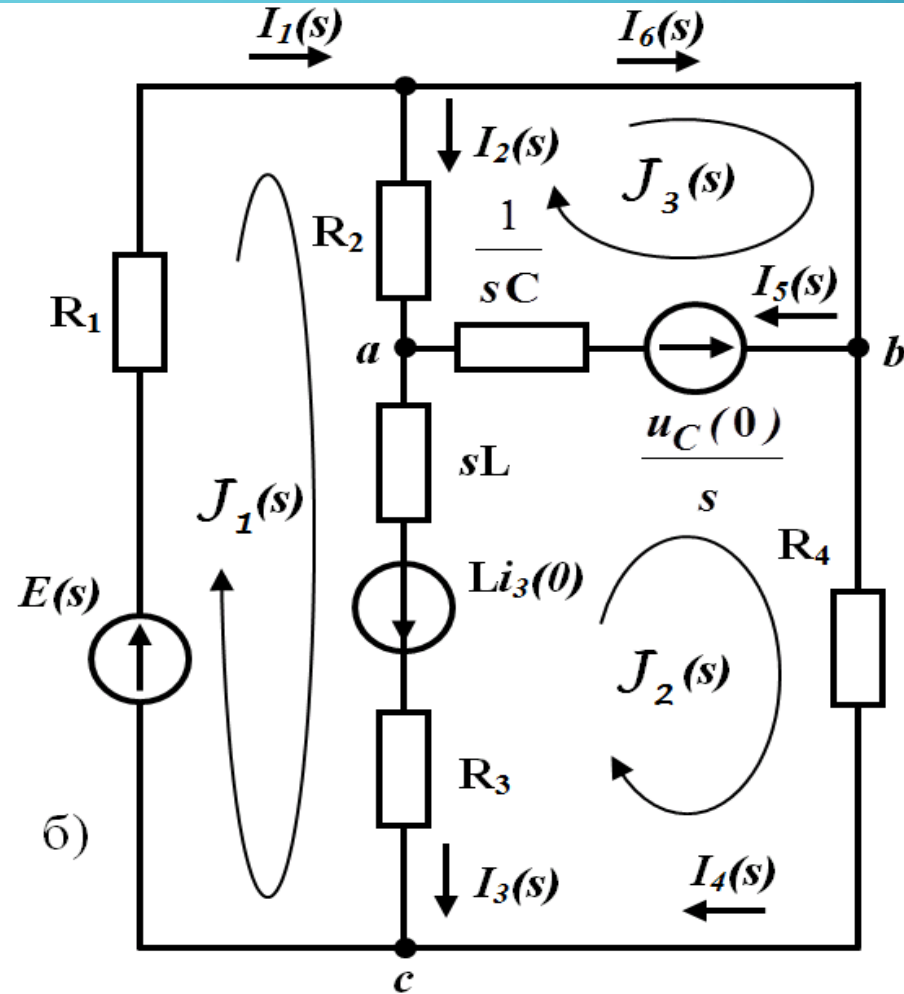

INDEPENDENT WORK

Complete an operator substitution scheme for the proposed circle

