

# VINNITSA NATIONAL AGRARIAN UNIVERSITY

Department of General Engineering Sciences and Labour Safety



## CALCULATION OF INITIAL AND FINAL STEADY STATES

by Associate Professor V. Hraniak



# Transients

**The time-varying currents and voltages resulting from the sudden application of sources, usually due to switching.**

**By writing circuit equations, we obtain integrodifferential equations.**

# The causes of transients:

## 1. Energy storage elements


-inductors and capacitors

$u_C, i_L$  change gradually;

## 2. Changing circuit, such as switching source.



# INITIAL STATE AND STEADY STATE

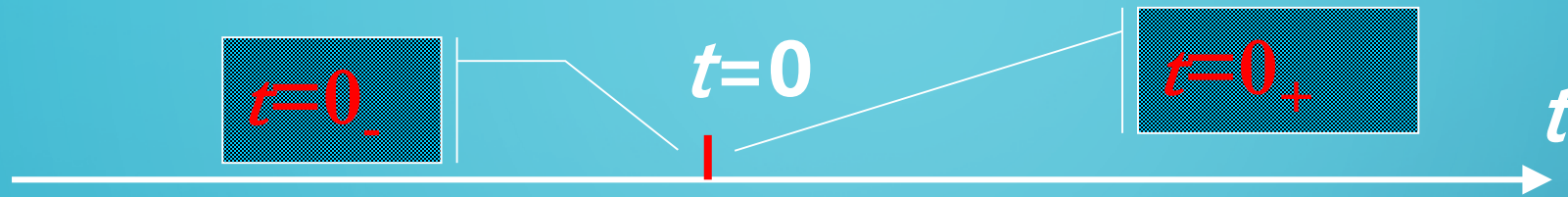

Assume changing circuit when  $t=0$ , then  $t=0-$  is end point of old steady state;  $t=0+$  is the start point of transient state.

$$\begin{cases} W_L(0_-) = W_L(0_+) \\ W_C(0_-) = W_C(0_+) \end{cases}$$

**The law of  
changing circuit**

$$\begin{cases} i_L(0_-) = i_L(0_+) \\ u_C(0_-) = u_C(0_+) \end{cases}$$

From  $t=0-$  to  $t=0+$ ,  $i_L$ 、 $u_C$   
change continuously.

# DC STEADY STATE RESPONSE

The steps in determining the forced response or steady state response for *RLC* circuits with DC sources are:

1. Replace capacitances with open circuits.
2. Replace inductances with short circuits.
3. Solve the remaining circuit.



# HOW TO GET INITIAL VALUE

**Exercise 1: Assuming old circuit is in DC steady state before switch K is closed. How to get  $u_C(0+), i_R(0+)$ ?**

**Solution:**

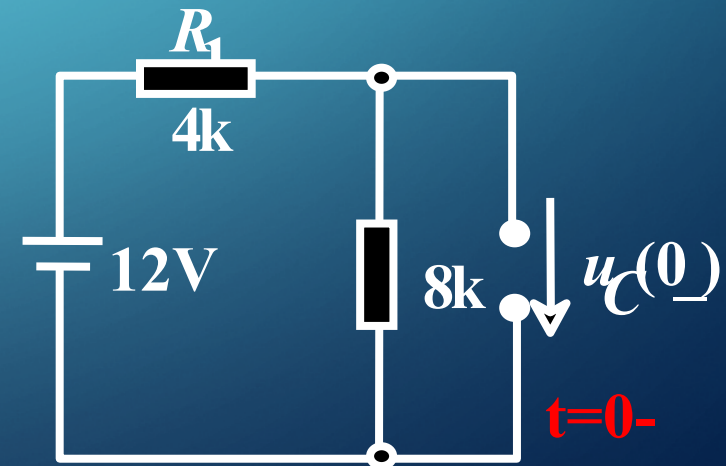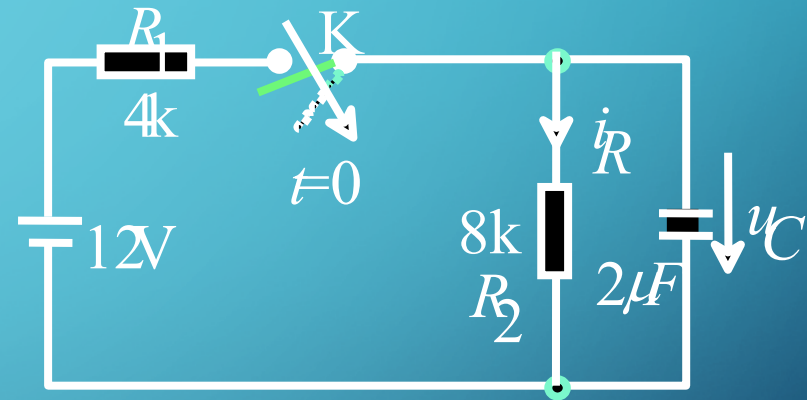
**When  $t=0-$ , capacitor is considered as open circuit, we get equivalent circuit.**

$$u_C(0_-) = \frac{8}{4+8} \times 12 = 8 \text{ V}$$






# How to get initial value

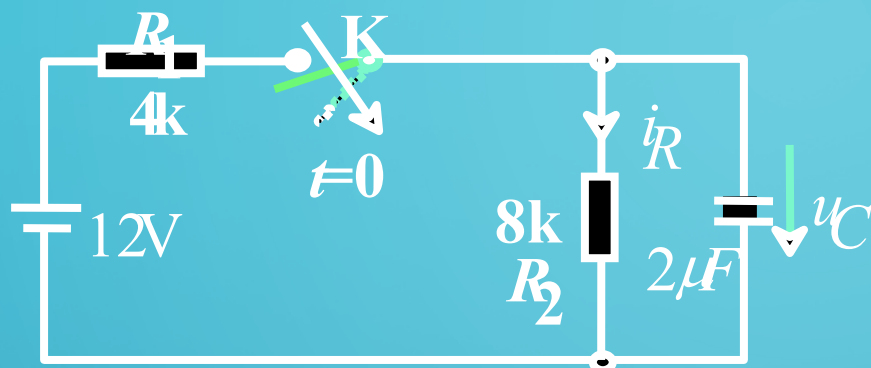


$$u_C(0_-) = \frac{8}{4+8} \times 12 = 8V$$

$$u_C(0_+) = u_C(0_-) = 8V$$

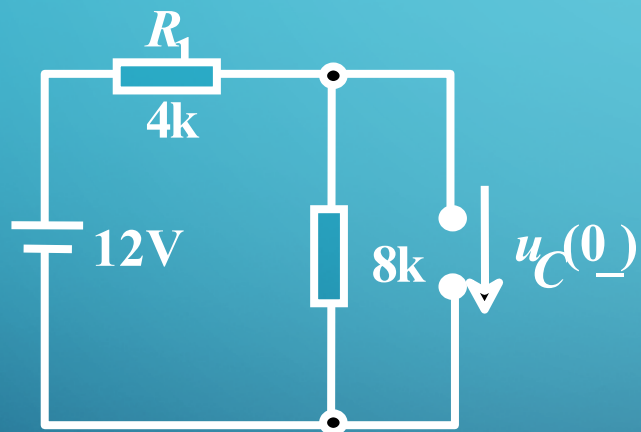substituting voltage source  
for  $u_C(0_+)$


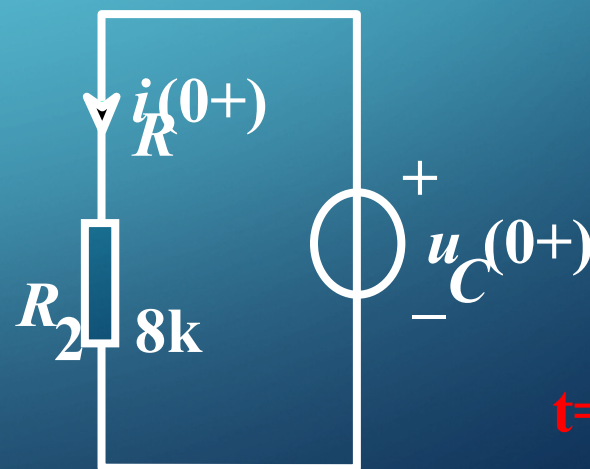
$$i_R(0_+) = \frac{u_C(0_+)}{R_2} = \frac{8}{8} = 1mA$$



$t=0_+$

**Example** Find steady-state values of  $v_x$  and  $i_x$  in this circuit for  $t \gg 0$ .


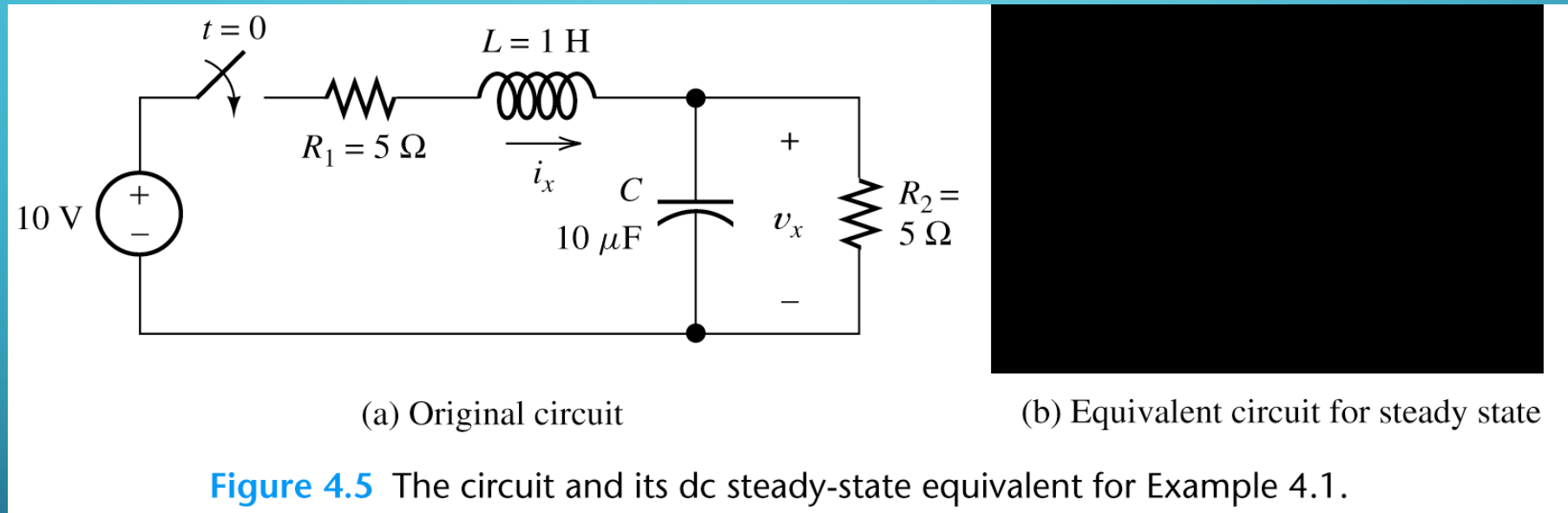


Figure 4.5 The circuit and its dc steady-state equivalent for Example 4.1.

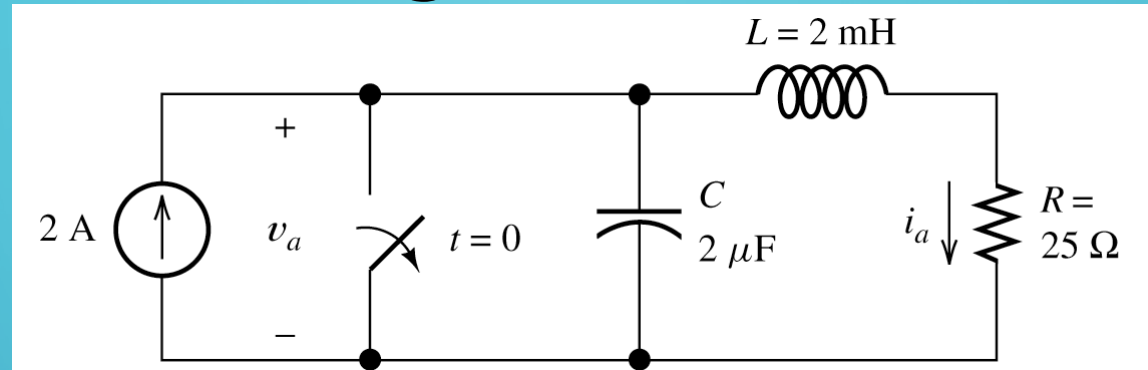
**Answer:  $v_x = 5\text{V}$ ,  $i_x = 1\text{A}$   $t \gg 0$**



## Exercise 4.3 Find steady-state values of labeled currents and voltages for $t \gg 0$ .



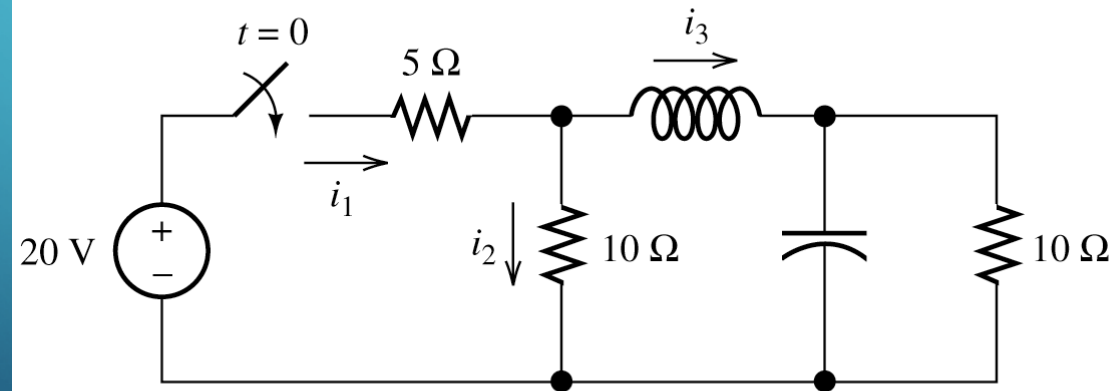**Answer:  $v_a = 50\text{V}$ ,  $i_a = 2\text{A}$**



(b)

**$i_1 = 2\text{A}$ ,  $i_2 = 1\text{A}$ ,  $i_3 = 1\text{A}$**

Figure 4.6 Circuits for Exercise 4.3.



# HOW TO GET INITIAL VALUE

**Exercise 1: Assuming old circuit is in DC steady state before switch K is closed. How to get  $u_C(0+), i_R(0+)$ ?**


**Solution:**

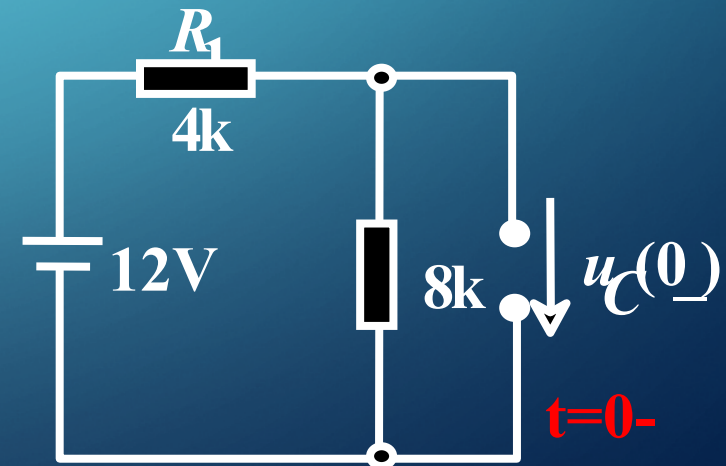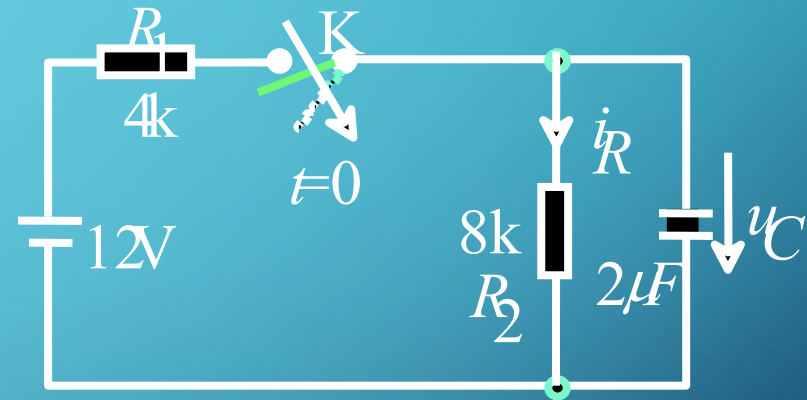**When  $t=0-$ , capacitor is considered as open circuit, we get equivalent circuit.**

$$u_C(0_-) = \frac{8}{4+8} \times 12 = 8 \text{ V}$$




# How to get initial value

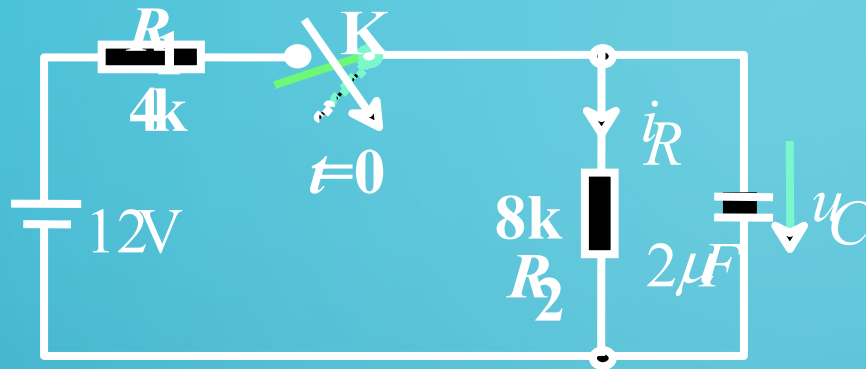


$$u_C(0_-) = \frac{8}{4+8} \times 12 = 8V$$

$$u_C(0_+) = u_C(0_-) = 8V$$

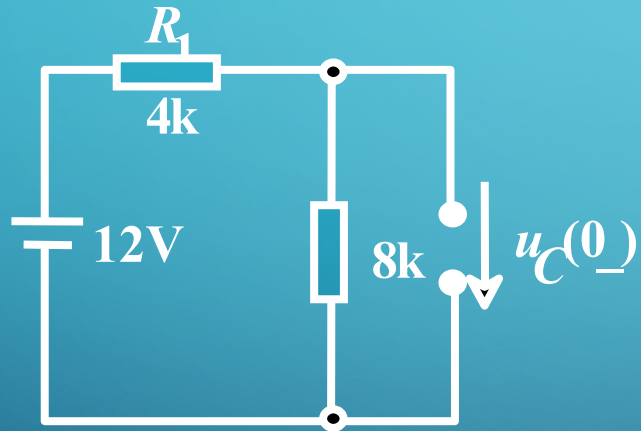substituting voltage source  
for  $u_C(0_+)$


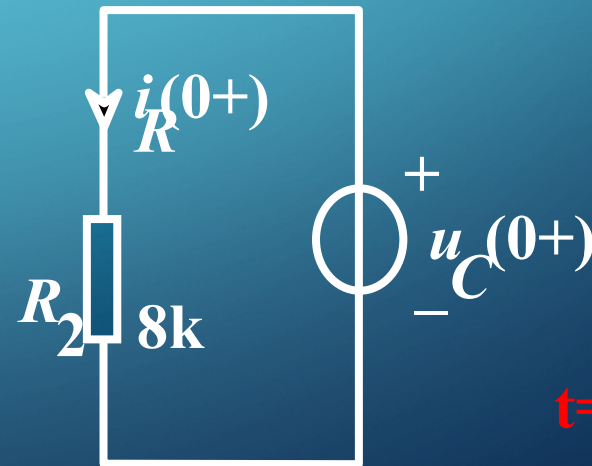
$$i_R(0_+) = \frac{u_C(0_+)}{R_2} = \frac{8}{8} = 1mA$$




$t=0_+$



# How to get initial value

**Exercise 2: Given by  $R_1=4\Omega$ ,  $R_2=6\Omega$ ,  $R_3=3\Omega$ ,  $C=0.1\mu\text{F}$ ,  $L=1\text{mH}$ ,  $U_S=36\text{V}$ , switch  $S$  is closed for a long time.**

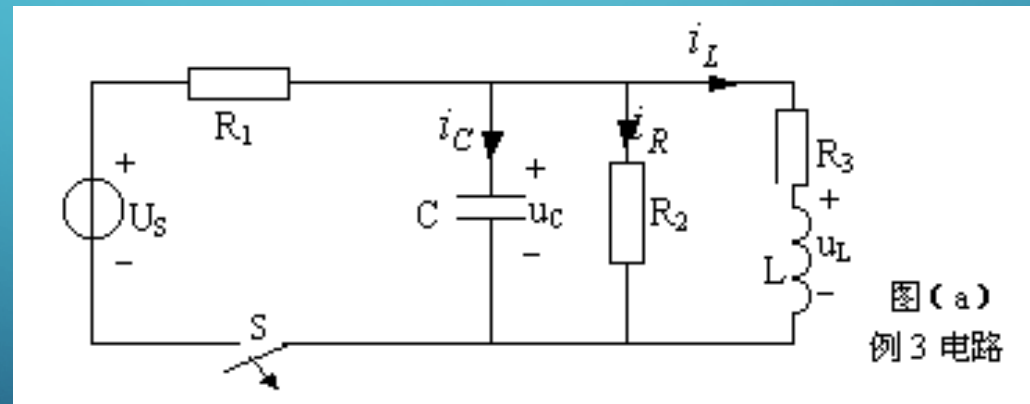**Open the switch  $S$  when  $t=0$ , how to get the initial values of all elements?**



# How to get initial value

**Exercise 3:**  $E=150\text{ V}$   $R1=5\ \Omega$   $R2=8\ \Omega$   $R3=7\ \Omega$

**How to get the initial and final values of all elements?**

